

# **Analog Front End Design for In-Vitro Diagnostic Applications**

**Andrew Wallace**

**Medical Systems Engineer**



**TEXAS INSTRUMENTS**

# In Vitro Diagnostic Equipment Landscape

|   |   |  | Key Technology Blocks   |
|---|---|--|---|
|   | END EQUIPMENT                             | CLINICAL USE   | KEY TECHNOLOGY BLOCKS   |
| Blood/Cell/<br>Fluid Analysis           | Chemistry/<br>Gas Analyzer                | -Diabetes<br>-Lipid Panel<br>-Lung Function  | -Electrochemical Sensing Front End<br>-Precision Optical Signal Path  |
|   | Hematology<br>Analyzer/<br>Flow Cytometer | -Complete Blood<br>Count (3/5 part)<br>- Cell Analysis                             | -Precision Optical Signal Path<br>-High Speed Signal Path<br>-Impedance Method (Coulter)<br>-Motor Automation |
|   | Immunoassay                               | -Antibody/Virus<br>-Pregnancy<br>-Drug/Doping<br>-Bacteria<br>-Cardiac<br>-Hormone | -Motor Automation<br>-Precision Optical Signal Path   |
| Molecular/<br>Genetic<br>Identification | Molecular<br>Analyzer                     | -Virus/Bacteria<br>Identification  | -Precision Optical Signal Path<br>-TEC Controller<br>-Motor Automation  |
|   | DNA Sequencer                             | -Genetic<br>Sequencing<br>-Cancer Genetics<br>-Prenatal                            | -TEC Controller<br>-Motor Automation  |

- **Precision Optical** – Precision measurement of charge or current from an opto-electronic receiver such as a photodiode is common in IVD. Many technologies such as PCR or Immunoassay systems use an assay or reagent to create a fluorescent or color change in a sample that will indicate the presence of a specific chemical or marker.
- **High Speed Optical**– In some cases, such as flow cytometry, the bandwidth requirements for light analysis can extend to several hundred Megahertz, requiring wide bandwidth amplifiers and Analog-to-Digital Converters (ADC).
- **Thermoelectric Cooling (TEC)** – Temperature measurement and control is essential for accuracy and fundamental for technologies such as PCR, where temperature cycling is required for sample analysis.  
**Electrochemical Sensing Front End** – Classic chemical measurement techniques are required for systems such as Blood Gas Analyzers, where voltage (potentiometry) or current (amperometry) measurements are needed for PH, CO<sub>2</sub>, Glucose and hundreds of other elemental quantities.
- **Motor Automation** – Motors play a key role in large lab-grade diagnostic equipment such as immunoassay analyzers, where sample throughput is critical.

# Agenda


- In Vitro Diagnostics Subsystems
  - Precision Optical
  - High-Speed Optical
  - Impedance Spectroscopy
  - Thermoelectric Cooling
  - Electrochemical Sensing
  - Motor/Motion Control

# Precision Optical


# Precision Optical: Overview

## Block Diagram

### Integrated

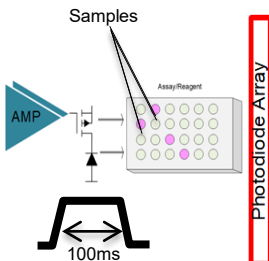


Photodiode Array

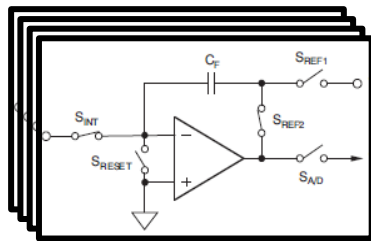

20bit ADC

DDC112/4/8.. Up to 256 ch

### Discrete

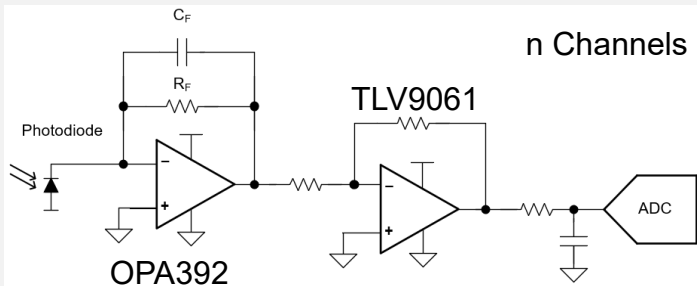

## System Design Challenge




**Design Challenge:** Accurate detection of very low light levels is needed in NAAT to measure the instant (quantification cycle, Cp) at which the fluorescence emission exceeds a given threshold, right above the noise.

**Solution:** The DDC11x integrates all the signal between two instants in time delivering directly the answer (all emitted photons). The low noise and high accuracy (low I<sub>bias</sub> and drifts) and integration of the full signal chain (TIA and ADC) saves space and hides the design complexity for designers, reducing time to market and lowering risk.

## Key Devices + Collateral


| Parameter      | Integrated  | Discrete   |
|----------------|---|--|
| GPN            | <a href="#">DDC112</a> (2 channels)<br><a href="#">DDC114</a> (4 channels)<br><a href="#">DDC118</a> (8 channels)<br><a href="#">DDC232</a> (32 channels)   | <a href="#">OPAx392</a> Low I <sub>B</sub> , Low noise precision amplifier<br><a href="#">TLV9061</a> Low I <sub>B</sub> , tiny general purpose amplifier<br><a href="#">ADS7066</a> 16ch SAR ADC<br><a href="#">ADS124S08</a> 24 bit ΔΣ ADC             |
| Description    | Integrates all current between two instants in time + 20b ADC <ul style="list-style-type: none"><li>Adjustable full scale range from 6.25pA to 3uA.</li><li>Fs: 1SPS to 100KSPS*</li><li>Up to 0.37fArms IRN</li><li>I<sub>B</sub>: 0.1pA typical</li></ul> | Discrete Transimpedance Analog Front End allows for customization and flexibility<br><br><a href="#">OPAx392</a> has I <sub>N</sub> : 40fA/rtHz, I <sub>b</sub> : 10fA, GBW: 13MHz<br><a href="#">ADS7066</a> 16 bit, 8 ch, F <sub>s</sub> up to 250kSPS |
| MPM Collateral | <ul style="list-style-type: none"><li><a href="#">DDC11xEVM-PDK Eval Board</a></li><li><a href="#">In-Vitro Diagnostics EERD</a></li></ul>  |  |
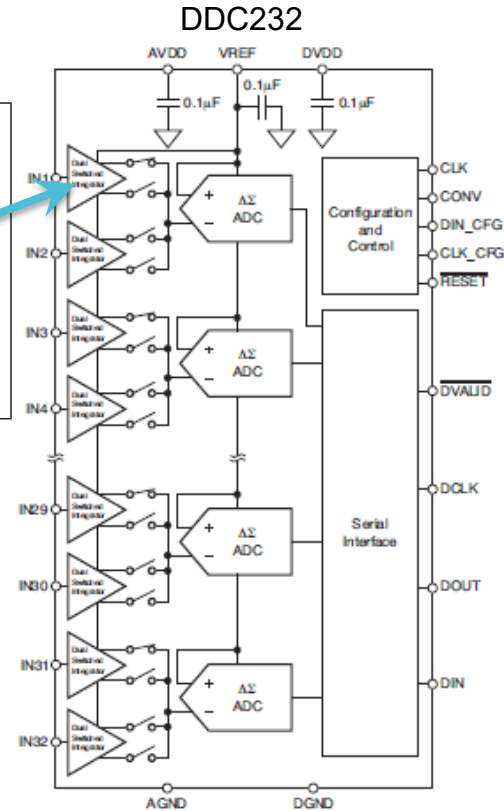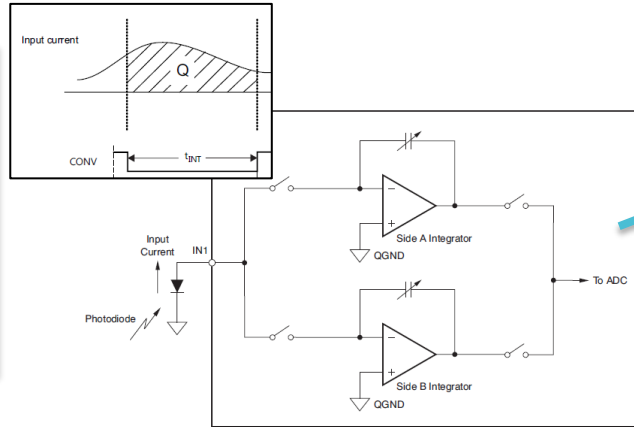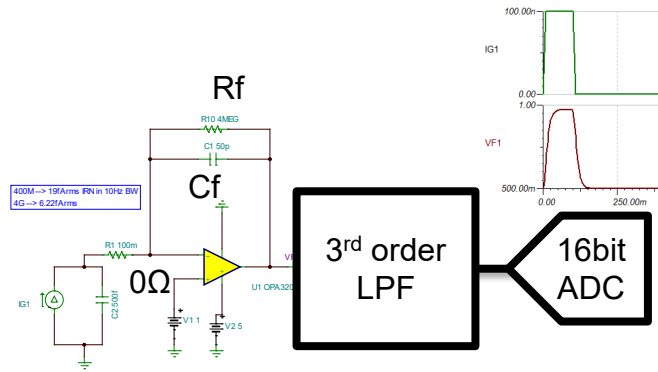
# Precision Optical: Integrated Solution (DDCx)



1. Large number of channels (from 2 to 256 channels fully integrated solution, including ADC).
2. Integration for total (or average) signal between two instants in time.
3. Programmability for different gain or bandwidth settings. Difficult to implement discretely and obtain excellent performance.
4. Easy of design and use. No calibration required in many cases. System performance reflected on the datasheet.
5. Relatively slow signals (~3KSPS max...). Integration BW ~MHz.
6. Relatively small currents ~1uA max. (There are techniques to extend the range but not out of the box and degrade performance).
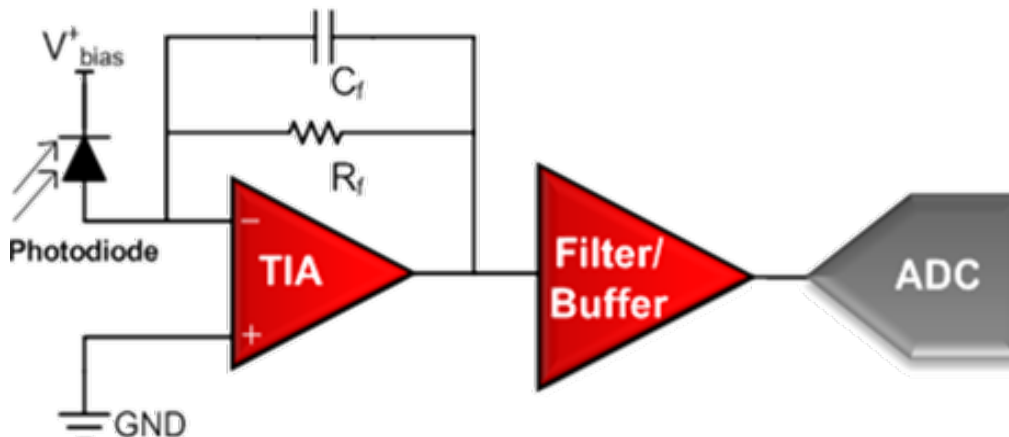
# Precision Optical: Electronic Signal Chain




1. **Transimpedance Amplifier (TIA):** converts current, generated by a photodiode, into voltage that drives the FDA for a differential input ADC. Must be low  $I_p$  and low  $I_n$  such as [OPAx392](#))
2. **Filter/Buffer:** used to drive ADC input. Can also be used for additional filtering/gain. Could be Buffer/Amplifier ([OPAx392](#)/[TLV9061](#)) for single-ended ADC or FDA ([THS4551](#)) for differential ADC.
3. **ADC:** multiple channels at high resolution are often required. Could be SAR ([ADS7066](#)) or Delta-Sigma ([ADS124S08](#)) architecture depending on timing requirements.

# Precision Optical: Schematic
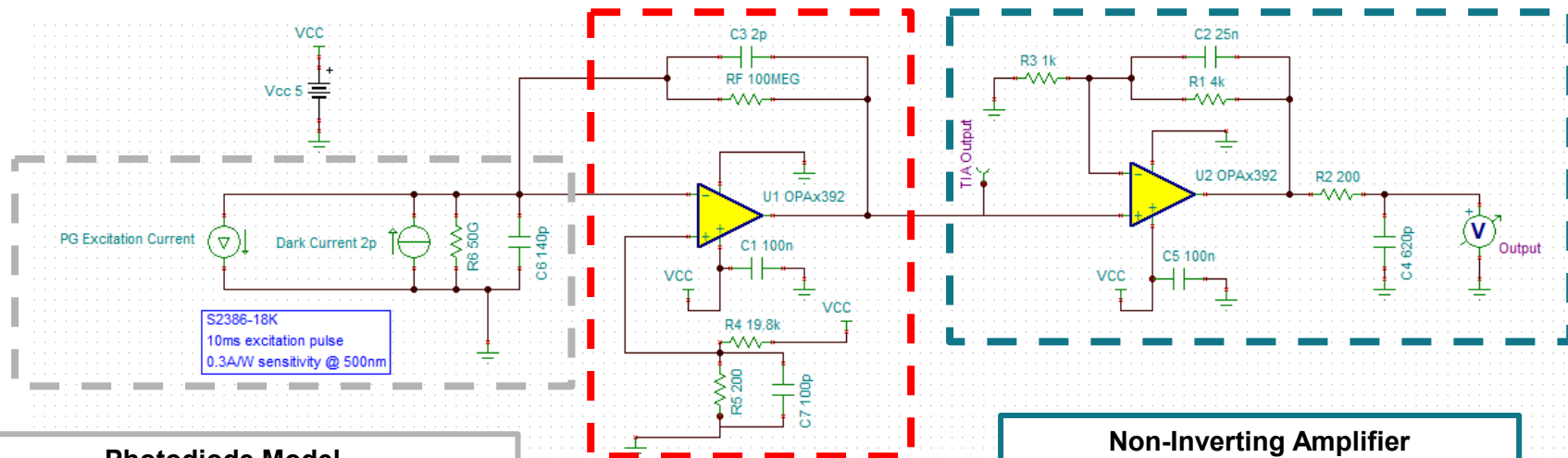
## Specifications

- **Excitation Pulse:** 10ms pulse, 32Hz
  - **Current Range:** ~0.476pA to 9.4nA
  - **Resolution:** 14.27bits
  - **Supply Voltage:** 5V single rail
- \*Passive components can be adjusted for various excitation range and timing requirements



### Photodiode Model

#### S2386-18K Photodiode

- Low Noise Eq. Power ( $6.8 \times 10^{-16}$  W/rtHz)
- Low dark current (2pA),
- Good sensitivity (0.3A/W at 500nm)

### TIA

#### OPA2392 Precision Op Amp

- Low  $I_n$  (4.0 nV/ $\sqrt{\text{Hz}}$ ),
- Low  $I_b$  (10fA)

### Non-Inverting Amplifier

#### OPA2392 Precision Op Amp

- High GBW (13MHz)
- Smaller BOM using 2<sup>nd</sup> channel



# Precision Optical: Sensitivity

$$I_{\max} = \frac{V_{\max\_swing}}{R_F \times G_{NIA}} = \frac{4.70V}{500M} = 9.4nA$$

$$\text{Optical Sensitivity} = \frac{V_{n-out}}{R_F \times G_{NIA}} (rms) \times 6 = \frac{266.8uArms}{500M} \times 6$$

$$= \mathbf{3.19pA} \text{ (0.476pA with 50 sample averaging (6.8ksps))}$$

$$\text{Dynamic Range} = \frac{9.4nA}{4.41pA} = 2.2k$$

$$= \mathbf{11.1bits} \text{ (14.27bits with 50 sample averaging (6.8ksps))}$$

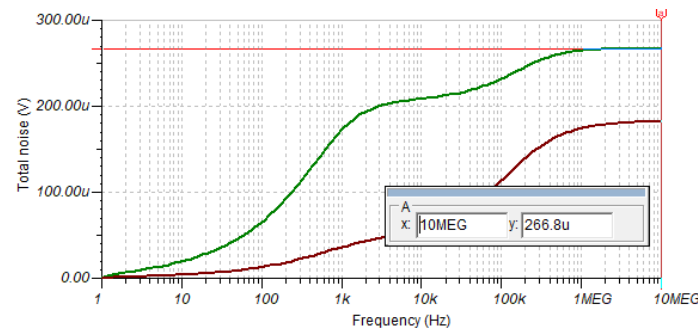
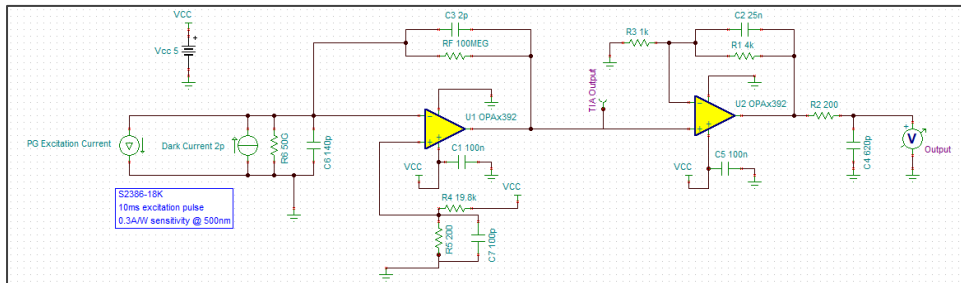


Figure 2. Total Noise vs. Frequency

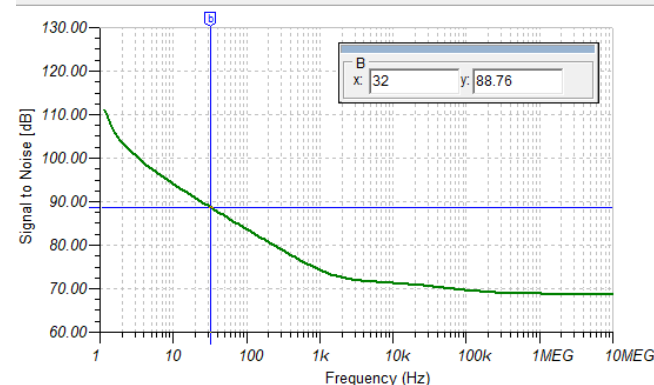


Figure 3. SNR at 32Hz input

$G_{NIA}$  = Gain of Non-inverting amp

# Precision Optical: AC Performance

$$\text{Settling Time (to 16 bits)} \cong 12 \times \sqrt{\tau_{TIA}^2 + \tau_{NIA}^2} = 2.68\text{ms}$$

$$F_{-3\text{dB}} = 670\text{Hz}$$

$$\text{Phase Margin} = 88.7^\circ$$

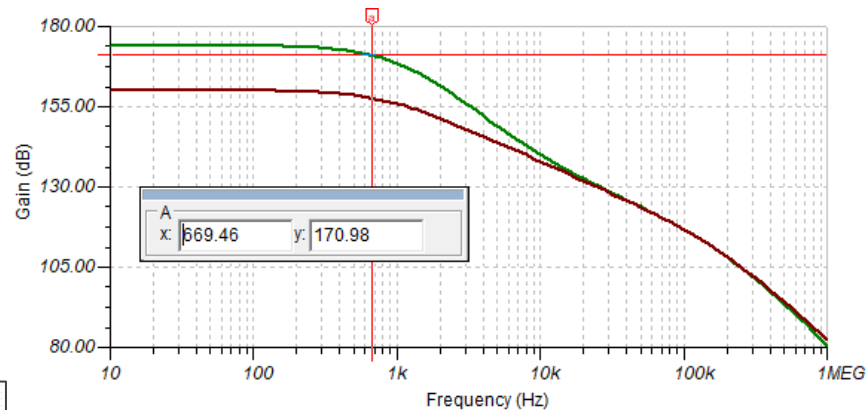
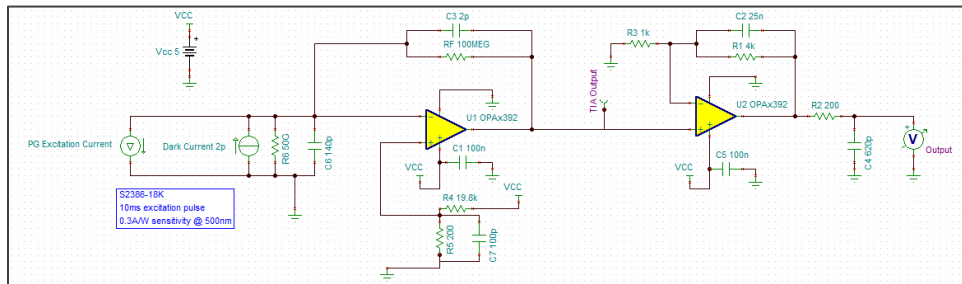


Figure 1. AC Transfer Characteristic

## Precision Optical: Accuracy

Error:



$$(\text{OPA392 } V_{OS})(\text{max}) \rightarrow 10\mu A \times 5 = \mathbf{0.05mV}$$

$$(\text{OPA392 } I_B)(\text{max}) \rightarrow 0.8pA \times 500M = \mathbf{0.4mV}$$


$$(\text{Dark Current})(\text{max}) \rightarrow 2pA \times 500M = \mathbf{1mV}$$

*(Resistors)(0.1% tolerance)* → **12.9mV**
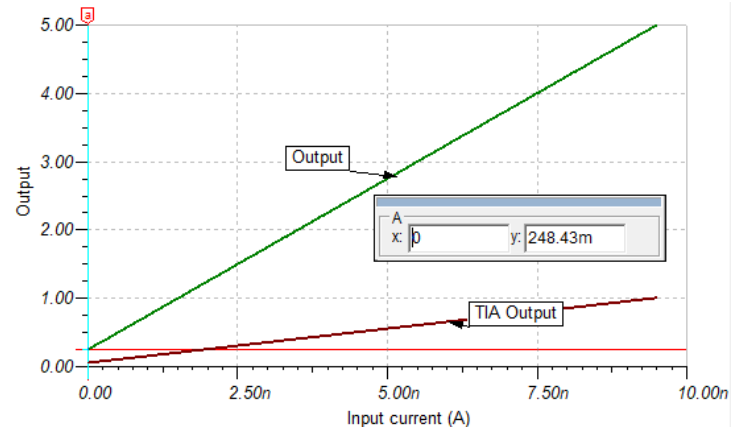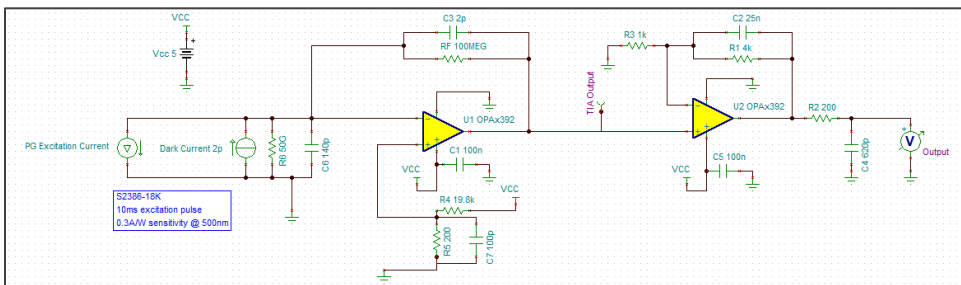
$$Accuracy = 1 - \frac{Error \text{ (worst case)}}{Full \text{ Scale Range}} = 1 - \frac{12.9\text{mV}}{4.95\text{V}} = \mathbf{0.997}$$




#### Figure 4. DC Transfer Characteristic

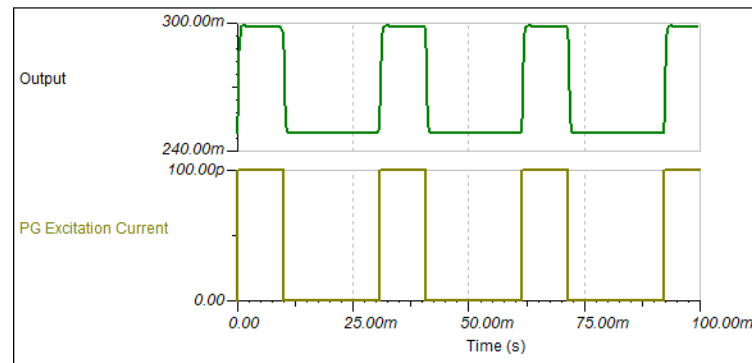

**Figure 5. Transient Response 10ms 100pA pulse @32Hz**


# High Speed Optical

# High Speed Optical: Optics and Sample

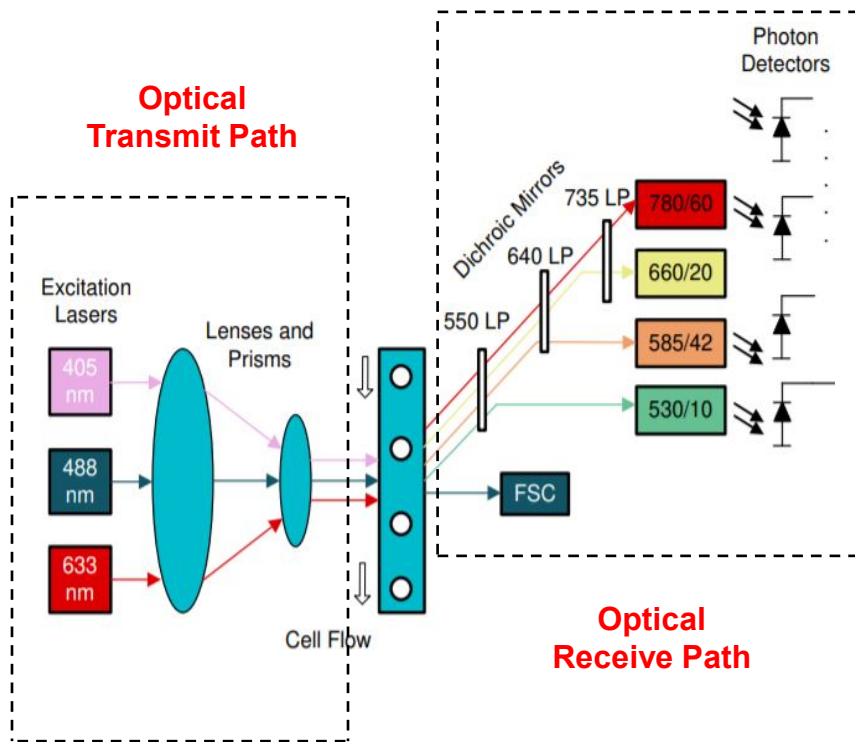





1. **Excitation Lasers:** Lasers are utilized as coherent, focused excitation light sources in order to excite fluorescent dyes and provide light for particle scatter measures.
2. **Lenses and Prisms:** The light that shines through the cell and moves in various directions is collected by multiple detectors (either photodiodes or photomultiplier tubes, PMT).
3. **Cell Flow:** A constant, stable pressure is applied to a tank of fluid (called sheath tank) holding an isotonic solution (similar to a saline solution) to create a laminar flow for the cells to move in a single stream through a cuvette.
4. **Mirrors and Filters:** Dichroic mirrors are used to dissect the polychromatic fluorescence that is overlapping (acting as physical filters) from each cell scattering.
5. **Photo Detectors:** The electronic signal chain contains the electronics to convert current from the PMT or photodiode into digital electronic signals for plotting.
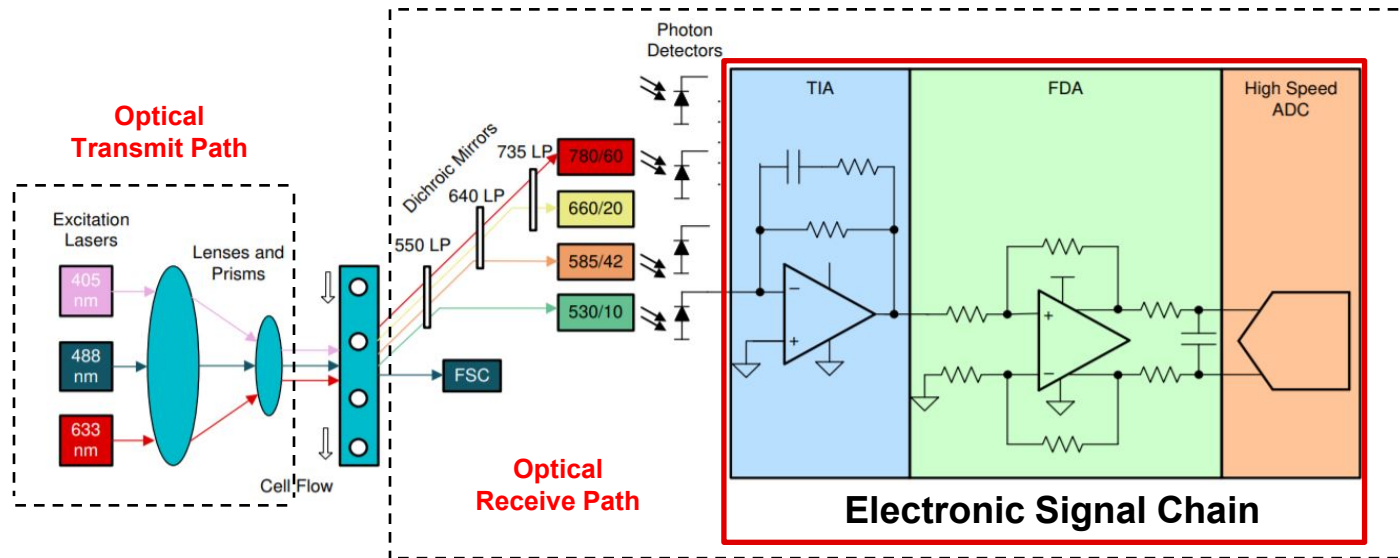
# High Speed Optical: Electronic Signal Chain



1. **Transimpedance Amplifiers (TIA):** converts current, generated by a photodiode, into voltage that drives the FDA for a differential input ADC.
2. **Fully Differential Amplifiers (FDA):** drives single ended to differential input Analog to Digital Converter (ADC) for high precision designs.

# High Speed Optical: Photodetectors
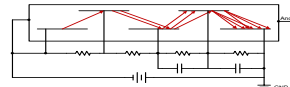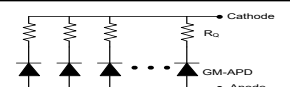
| Sensor  | Description  | Example Applications  | Rise Time       | Capacitance Range | Current Range           | Dark Current     |
|---|--|---|-----------------|-------------------|-------------------------|------------------|
| <b>Photodiode (PD)</b><br>                    | <ul style="list-style-type: none"> <li>PN or PIN junction photodetector with no gain</li> <li>Suitable for detecting bright forward light and side light scatter</li> </ul>  | <ul style="list-style-type: none"> <li>Chemistry Analyzer</li> <li>qPCR</li> <li>Optical Communication Systems</li> </ul>   | ~30ps-1 $\mu$ s | ~0.5pF-200pF      | ~10nA-100 $\mu$ A       | ~1pA-1nA         |
| <b>Avalanche PD (APD)</b><br>                 | <ul style="list-style-type: none"> <li>Similar in structure to a PIN PD, but has intrinsic gain due to use of different doping profiles</li> <li>Higher photosensitivity, responsivity and SNR compared to PD</li> </ul>   | <ul style="list-style-type: none"> <li>Flow Cytometry</li> <li>Lidar</li> <li>Optical Communication Systems</li> </ul>  | ~0.5ns-100ns    | ~1pF-150pF        | ~100nA-1mA              | ~1nA-50nA        |
| <b>Photomultiplier Tube (PMT)</b><br>         | <ul style="list-style-type: none"> <li>Vacuum tubes that contains a photocathode, anode, and multiple stages of dynodes in between for amplification</li> <li>Suitable for detection of very low light or low scattering signals down to single photons</li> </ul> | <ul style="list-style-type: none"> <li>Flow Cytometry</li> <li>Hematology Analyzer</li> <li>Spectroscopy</li> <li>Confocal Microscopy</li> <li>PET</li> <li>HEP</li> </ul>      | ~0.5ns-50ns     | ~0.1nF-10nF       | ~10 $\mu$ A-100 $\mu$ A | ~30pA-10nA       |
| <b>Solid-State Photomultiplier (SiPM)</b><br> | <ul style="list-style-type: none"> <li>Solid-State photomultiplier which contains a parallel combination of Geiger-mode silicon APD</li> <li>Responsivity levels similar to those of PMTs</li> </ul>   | <ul style="list-style-type: none"> <li>Flow Cytometry</li> <li>DNA sequencers</li> <li>Laser scan microscope</li> <li>PET Scanners</li> <li>Fluorescence measurement</li> </ul> | ~1ns-1 $\mu$ s  | ~50pF-1nF         | ~1 $\mu$ A-10mA         | ~10nA-10 $\mu$ A |

# High Speed Optical: TIA + FDA Simulation

1. Calculate the Feedback Resistance based on the desired Output Voltage and the Photo Detector's peak current

- Determine the Feedback Capacitance using feedback resistance and Photo Detector's signal bandwidth
- Determine Amplifier GBWP using total input capacitance, feedback resistance, and feedback capacitance
- TIA's feedback resistance dominates the TIA's output noise
- CMOS/FET Input TIA is preferred at higher resistance such as in the M $\Omega$


2. Use FDA to convert single ended to differential input to drive ADC

3. TIA's output noise from ADC's SNR in time domain

- Higher order filter can be added for noise reduction

4. Maximize ADC's input full scale for unipolar pulse

| Sensor | Rise Time   | Frequency Range | Capacitance Range | Input Current | Feedback Resistor at 2Vpp | Approx. GBW Range |
|--------|-------------|-----------------|-------------------|---------------|---------------------------|-------------------|
| PMT    | ~0.5ns-50ns | 100MHz – 500MHz | 1n                | 100 $\mu$ A   | 10k $\Omega$              | 5.5GHz            |

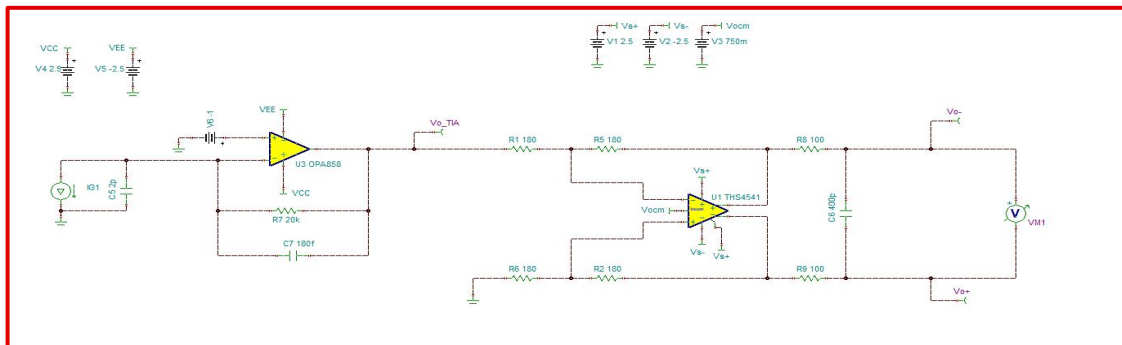



# Simulation Results: Photomultiplier Tube (PMT)

$$R_{Fmax} = \frac{V_{max\_swing}}{I_{max}} = \frac{1V}{100\mu A} = 10k\Omega$$




$$F_{-3dB} = \frac{0.35}{t_R} = \frac{0.35}{50ns} \approx 7MHz$$

$$C_F = \frac{1}{2\pi R_F F_P} = 2.27pF$$

$$GBP \geq \frac{C_{TOT} + C_F}{2\pi R_F C_F^2} = 5.5GHz$$

OPA858: 5.5GHz

OPA855: 8GHz

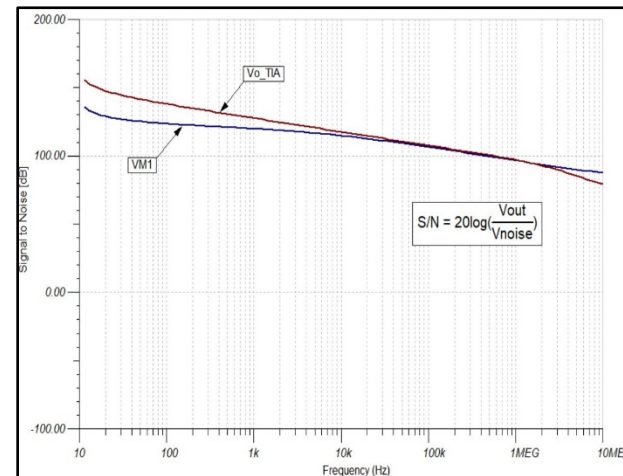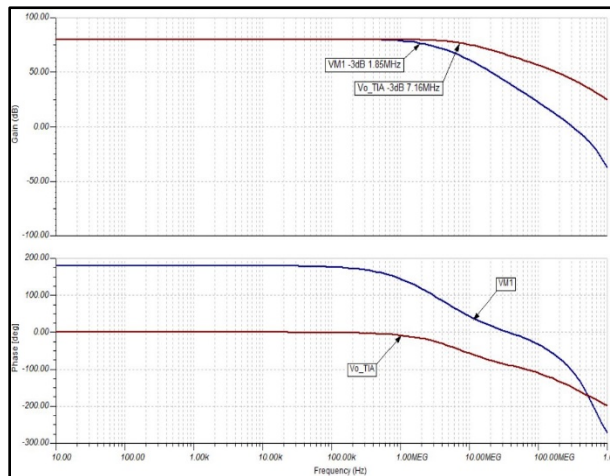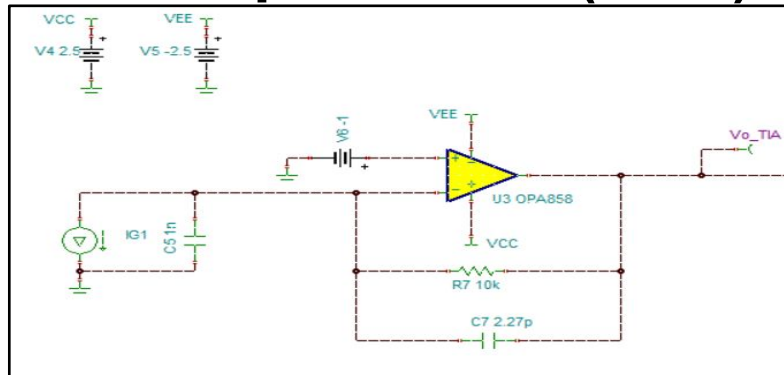


# Simulation Results: TIA Selection

| Sensor | Frequency Range  | Capacitance Range | Current Range | Feedback Resistor Range at 2Vpp | Approx. GBW Range | Example Transimpedance Amplifiers (TIA)   |
|--------|------------------|-------------------|---------------|---------------------------------|-------------------|---|
| PD     | 100kHz – 5000MHz | 0.5pF-200pF       | 10nA-100μA    | 10kΩ-100MΩ                      | 10MHz-100GHz      | <b>OPA855</b> : Low Noise, <b>8GHz</b> , Decompensated Bipolar-Input Amplifier<br><b>OPA857</b> : Low Noise, Fast Recovery Time, <b>6.8GHz</b> , Integrated TIA with Gain Control   |
| APD    | 10MHz - 1000MHz  | 1pF-150pF         | 100nA-1mA     | 1kΩ-10MΩ                        | 100MHz-10GHz      | <b>OPA858</b> : Low Noise, <b>5.5GHz</b> , Decompensated FET-Input Amplifier  |
| PMT    | 100MHz – 500MHz  | 0.1nF-10nF        | 10μA-100μA    | 10kΩ-100kΩ                      | 1GHz-100GHz       | <b>OPA818</b> : Low Noise, High Voltage, <b>2.7GHz</b> , Decompensated FET-Input Amplifier<br><b>OPA657</b> : High Precision, High Output Current, <b>1.6GHz</b> , Decompensated FET-Input Amplifier  |
| SiPM   | 1MHz – 100MHz    | 50pF-1nF          | 1μA-10mA      | 100Ω-1MΩ                        | 100MHz-10GHz      | <b>OPA856</b> : Low Noise, Wide Output Swing, <b>1.1GHz</b> , Bipolar-Input Amplifier<br><b>LMH32401</b> : Programmable gain, Differential Output ADC driver, Integrated TIA, Ambient Light Cancellation, 100mA Protection Clamp, <b>450MHz</b> (1, 4 Channels, Q100 Option)<br><b>OPA656</b> : High Precision, High Output Current, <b>230MHz</b> , FET-Input Amplifier<br><b>OPA810</b> : Low noise, RRIO, High Output Current, <b>70MHz</b> , FET-Input Amplifier (1, 2 Channels)<br><b>OPA607</b> : High Precision, <b>50MHz</b> , RRO, Decompensated CMOS Amplifier (1, 2 Channels)<br><b>OPA320</b> : High Precision, <b>20MHz</b> , RRIO, Zero-Crossover, CMOS Amplifier (1, 2 Channels) |

# High Speed Optical: Summary

## Block Diagram

### Flow Cytometry Front End

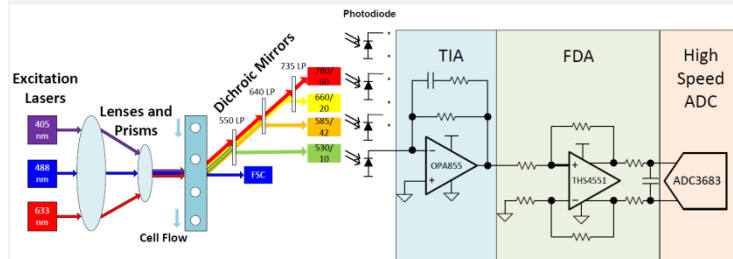

## System Design Challenge

**Design Challenge:** Multiple channels (24~48) running at high speed (40~125MSPS) and high resolution (14~18bits). Received signals are typically low magnitude in uAs and hence need low noise transimpedance amplifier, >50MSPS, and 16~18bit multi-channel ADCs.

**Solution:** 14~16bit/80~125MSPS 4-8CH ADC family provide low power, high SNR, digital decimation/demodulation and advanced interfaces, eg. LVDS (1Gbps) and JESD204B (12.8Gbps). OPA818 provides low-noise current-to-voltage conversion. THS45xx acts as fully differential buffer for ADCs.

## Key Devices + Collateral

| Parameter      | 1~2CH Devices  | 4~16CH TI devices  |
|----------------|--|--|
| GPN            | <a href="#">OPA855</a><br><a href="#">OPA320</a><br><a href="#">THS4551</a><br><a href="#">ADC3683</a>   | <a href="#">LMH32404</a> / <a href="#">OPA2607</a><br><a href="#">OPA2320</a> / <a href="#">THS4552</a><br><a href="#">ADC3443</a>                                       |
| Description    | TIA + FDA + 1~2 channel,<br>65~80 MSPS, 16~18 bit ADCs   | TIA + FDA + 4~16 channel,<br>65~125 MSPS, 14~16-bit ADCs   |
| AFE Collateral | <ul style="list-style-type: none"><li><a href="#">Flow Cytometry Signal Chain</a></li><li><a href="#">Flow Cytometry Simulation TI.com</a></li><li><a href="#">Photodiode Amplifier Design</a></li></ul> | <ul style="list-style-type: none"><li><a href="#">Why use oversampling</a></li><li><a href="#">Understanding JESD204B Subclasses and Deterministic Latency</a></li></ul> |


# Impedance Spectroscopy

# Impedance Spectroscopy: Overview

**Design Challenge:** Many Impedance Spectroscopy applications require customized excitation parameters while delivering measurements that have high SNR and minimized phase shift. These parameters affect how accurately a system can be calibrated to deliver highly accurate test results.



**Solution:** Impedance Spectroscopy measurements are applicable in many systems, ranging from blood test equipment to battery impedance testers. A discrete solution allows for a highly flexible solution that can deliver very low phase shift, and high SNR measurements using a wide range of excitation amplitudes and frequencies.

## Key Devices + Collateral

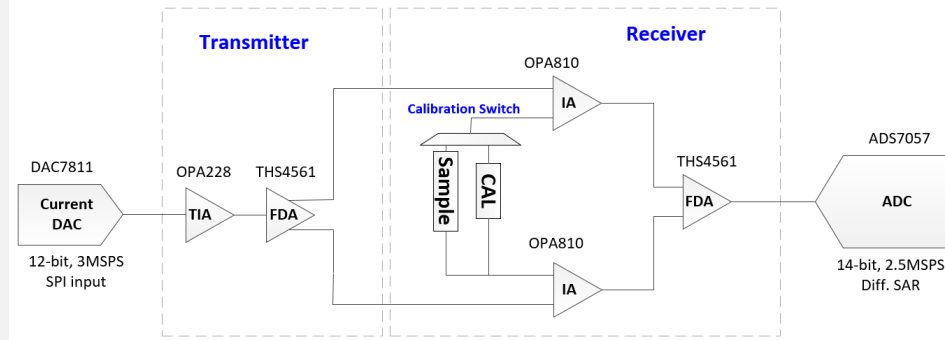

| Parameter      | DAC  | Amplifiers  | Precision ADC                        |
|----------------|--|---|--------------------------------------|
| GPN            | <a href="#">DAC7811</a>  | <a href="#">THS4561</a> , <a href="#">OPA810</a> ,<br><a href="#">THP210</a> , <a href="#">OPA228</a> | <a href="#">ADS7057</a>              |
| Description    | 12-bit High Speed DAC with low noise for excitation signal generation  | Precision High-Bandwidth Amplifiers to maintain signal integrity while reducing signal phase shift    | 14-bit, 2.5MSPS Differential SAR ADC |
| MPM Collateral | <a href="#">Impedance Spectroscopy Simulation (Differential)</a><br><a href="#">Impedance Spectroscopy Simulation (Single-Ended)</a> |   |                                      |
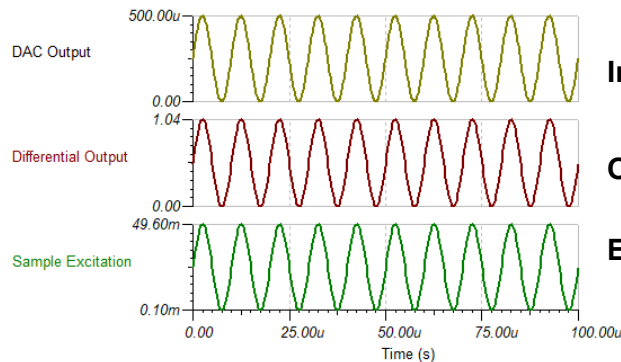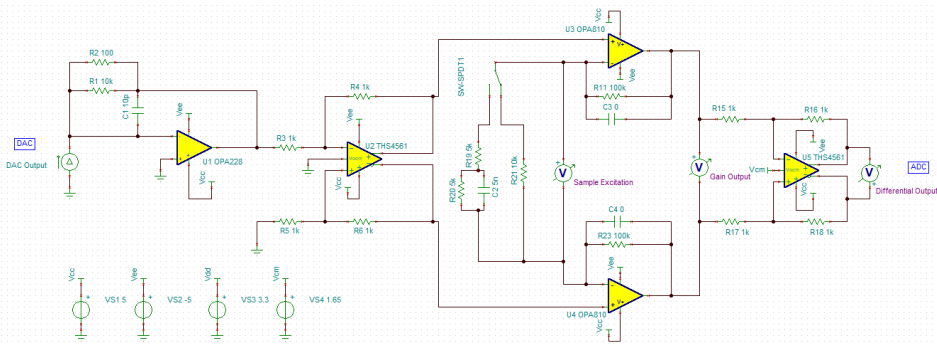
# Impedance Spectroscopy: Simulation – Differential



**Input Signal = 500uA p-p**


**Output Signal = 192.3 mV p-p**

**Excitation= 49.5mV p-p**
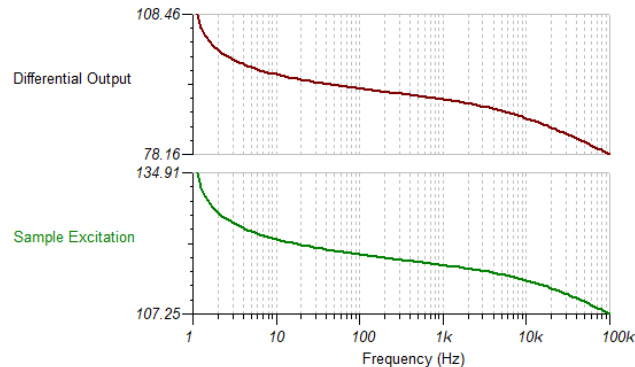
## Original Specifications



- **Excitation Frequency:** 10mHz-100kHz
- **Frequency resolution:** 12bit 2.5MSPS DAC
- **Excitation Voltage:** 1mV-200mV.
- **Impedance Range:** 1ohm-10Mohm
- **Number of electrodes:** Dual electrode probe, such as a coaxial probe

[Impedance Spectroscopy Simulation \(Differential\) TI.com Link](#)



**SNR @ output = 78.16dB @ 100kHz**
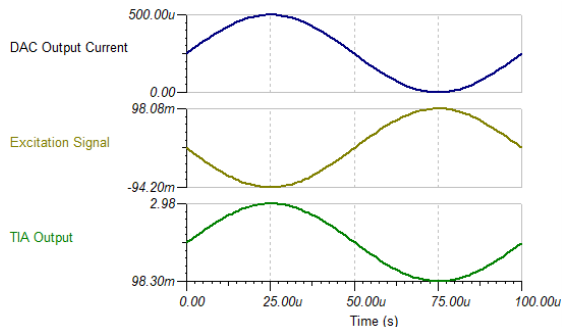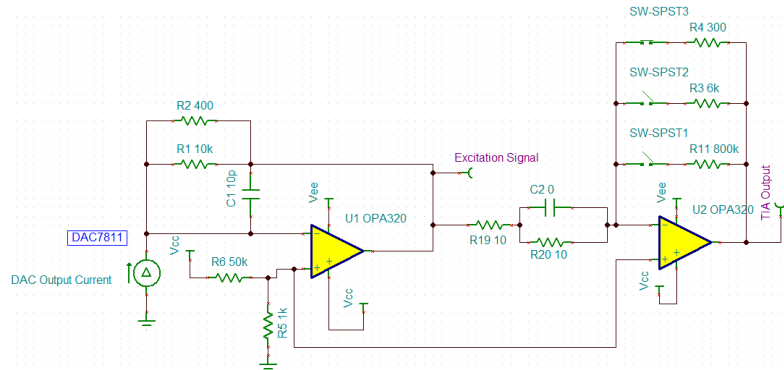
# Impedance Spectroscopy: Simulation – Single-Ended



**Input Signal = 500uA p-p**


**Excitation = 192.3 mV p-p**

**Output Signal = 2.88V p-p**
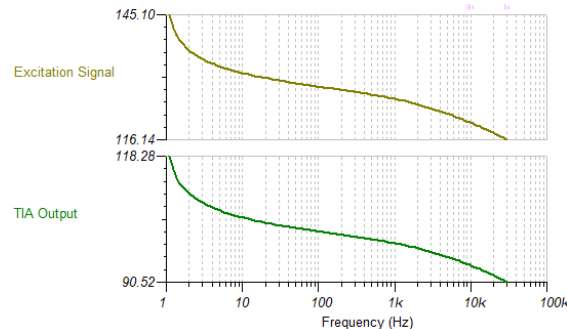
## Original Specifications

- **Excitation Frequency:** 10mHz-30kHz
- **Frequency resolution:** 12bit 2.5MSPS DAC
- **Excitation Voltage:** 100mV-2V.
- **Impedance Range:** 1ohm-1Mohm
- **Number of electrodes:** Dual electrode probe, such as a coaxial probe

[Impedance Spectroscopy Simulation \(Single-Ended\) TI.com Link](#)



**SNR @ output = 90.52dB @ 30kHz**

**OPA3S328 – 1pA  $I_B$ , high precision, high speed (40MHz), zero-crossover RRIO with Integrated Switches**

# AFE4500: A Device Overview

## Analog Front End for Voltage, Current and Impedance Sensing

### Features

- Simultaneous signal acquisition from different LED sensors at different data rates, high input impedance INA and impedance.
- 24 highly flexible sampling phases.

#### OPTICAL SIGNAL CHAIN:

##### LED Receiver:

- 2 parallel receivers (two sets of TIA/ filter)
- Individual DC Offset Subtraction DAC at each TIA Input with 8-bit per-phase control , Range ~16 $\mu$ A-256  $\mu$ A
- Automatic DC cancellation and dynamic LED DC cancellation at TIA input
- Trans-impedance Gain: 3.7 k $\Omega$  to 1 M $\Omega$

##### LED Transmitter:

- 8-Bit Programmable LED Current with range adjustable from 25 mA to 250 mA
- Mode to fire two LEDs in parallel with independent per-phase current control
- Support of 8 LEDs in Common Anode configuration for Multi-Wavelengths


#### HIGH INPUT IMPEDANCE VOLTAGE CHANNEL:

- Sampling up 2 kHz
- Input noise (0.5-150 Hz): 0.75  $\mu$ V at 1 kHz data rate
- Programmable INA gain: 2,5,5, 11, 21
- Integrated LPF, High pass filter: 0.4 Hz corner set by 10 $\mu$ F external capacitor, quick saturation recovery
- Bias voltage output, AC and DC sensor lead-off detect, lead-on detection.
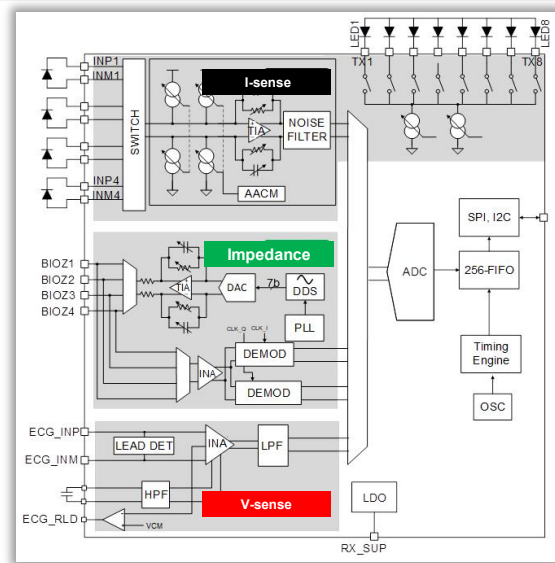
#### IMPEDANCE SIGNAL CHAIN:

- Multi-frequency impedance Analysis - up to 250 kHz excitation frequency
- Complex (I,Q) Tetrapolar impedance measurement
- Sine-wave excitation with a 7-bit DAC and programmable amplitude
- Noise of 40 m $\Omega$ pp over a 0.1Hz to 4Hz Bandwidth.
- Calibration scheme to compensate for electrode impedance
- Automatic impedance Calibration

- Supports external clock and internal oscillator modes
- Option to acquire data synchronized with a system master clock
- Option to Daisy chain 2 AFEs to acquire signals from 2x the number of LEDs and PDs synchronously
- FIFO with 256-sample Depth
- SPI, I2C interfaces: Selectable by pin
- 3-mm  $\times$  2.6-mm DSBGA, 0.4-mm Pitch
- Supplies: Rx:1.7-1.9V (LDO Bypass); 1.9-3.6V (LDO Enabled), Tx:3-5.5V, IO:1.7-RX\_SUP





# Thermoelectric Cooling

# Thermoelectric Cooling: Overview

| Design challenge/problem statement   | Block diagram/schematic | Additional resources   |  |   |  |
|--|-------------------------|--|--|---|--|
| <ul style="list-style-type: none"><li>Thermoelectric Cooling is used in many different End Equipment's to provide precision temperature regulation of samples, light sources and system components.</li><li>These EE's have a range of requirements for power (15W-100W), efficiency, size and integration.</li><li>Implementation of a real time control loop that can add overhead to the main processor</li></ul>   |                         |  |  |   |  |
|  |                         | Driver   | Current Sense  | Temp Sense  |  |
| GPN  |                         | <a href="#">DRV8873</a><br><a href="#">DRV8432</a>   | <a href="#">INA260</a><br><a href="#">TMCS1101</a>                             | <a href="#">TMP117</a>  |  |
| Description  |                         | H-bridge motor drivers w/ low-pass filter to deliver high-efficiency bipolar drive   | Precision Current and Power Monitor With Low-Drift, Precision Integrated Shunt | 0.1°C Digital Temperature Sensor<br>Lower power and Lower cost than Class AA RTD Equivalent |  |
| Technical resources  |                         | <ul style="list-style-type: none"><li><a href="#">Driving a Peltier Element (TEC) Reference Design</a></li><li><a href="#">Low Power TEC Driver Reference Design</a></li></ul> |  |   |  |
| What differentiates this subsystem solution  | TEC in a System         |  |  |   |  |
| <ul style="list-style-type: none"><li>We have a wide range of proposals to meet customer needs depending on the system. We can implement integrated H-bridge drivers to deliver 2 to 4 channels at 15W-80W and &gt;85% efficiency. We can also provide solutions using a linear buck converter to provide single channel solutions at &gt;15W and &gt;95% efficiency.</li><li>The smart AFE (AFE539A4) allows customers to offload the real time control loop. This AFE uses a PID system in order to regulate the system to a set temperature point specified over I2C. This removes all needs of an interrupt or DMA based control system using their main controller.</li></ul> |                         |  |  |   |  |
|  |                         | Driver   | AFE  | Power MOSFET  |  |
| GPN  |                         | <a href="#">LM60430</a>  | <a href="#">AFE539A4</a>   | <a href="#">CSD17577Q3A</a>   |  |
| Description  |                         | 3.8-V to 36-V, 3-A, ultra-small synchronous step-down converter  | 10 bit Quad Smart AFE for closed loop regulation                               | 30 V N-Channel NexFET™ Power MOSFET<br>5.3mOhm R <sub>DSon</sub>                            |  |
| Technical resources  |                         | <ul style="list-style-type: none"><li><a href="#">Video Link</a></li></ul>   |  |   |  |

TI Confidential – NDA Restrictions

26

# AFE539A4: Device Overview

## 10 bit Quad Smart AFE – A new building block

### Features


- User programmable Nonvolatile Memory (NVM/EEPROM)
- I2C and SPI mode auto-detection
- Internal 1.22-V reference
- Hi-Z output during power-off condition
- GPIO pin configurable as LDAC/PRESET/SDO/PDN/ALARM
- 10-bit ADC mode for all channels
- Control logic that supports feed-forward and closed-loop control
- Voltage output with flexible configuration
  - 1 LSB INL and DNL, Gain of 1, 1.5, 2, 3 and 4
- Current output
  - 1 LSB INL (8-bit), 1 LSB DNL
  - Configurable output ranges
    - 0  $\mu$ A to 25  $\mu$ A,  $\pm 25$   $\mu$ A,  $\pm 125$   $\mu$ A,  $\pm 250$   $\mu$ A
- Wide operating range
  - Power supply: 1.8 V to 5.5 V
  - Temperature range: -40°C to +125°C
- Small packages
  - WQFN-16 (3x3)

### End-equipment

- Ethernet switches and routers
- Handheld medical devices, test & measurement equipment
- TEC
- Land mobile radio
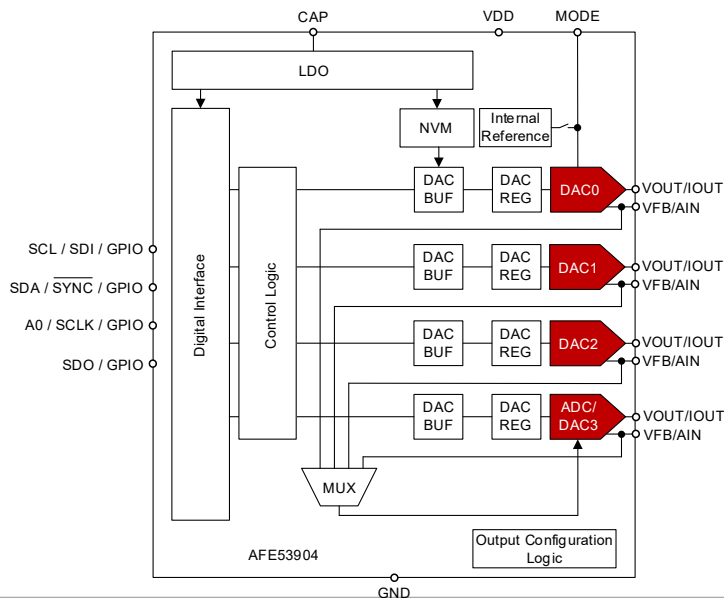
### Benefits

- High design-reuse with multiple digital interface and analog output options
- Set-and-forget mode operation off-loads housekeeping MCU/EC
- Autonomous mode provides logic to analog circuits without software
- Ultra-low power enables longer run-time for battery-operated applications




# Thermoelectric Cooling: TMP117 Benefits
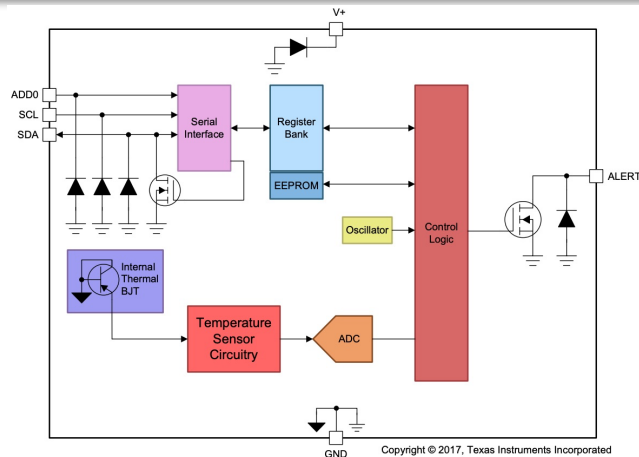
## TMP117 Advantages:

- Higher accuracy than Class AA RTD
  - $0.1^{\circ}\text{C}$  ( $-20^{\circ}\text{C}$  to  $50^{\circ}\text{C}$ ),  $-55^{\circ}\text{C}$  to  $150^{\circ}\text{C}$  operating range
- No calibration needed
- Simpler design with fewer components and less layout constraints
  - TMP117 includes ADC, I2C with interrupt, and EEPROM
- Significantly lower power than RTDs (TMP117:  $<9\mu\text{W}$  @ 1sps)




*TMP117 Packages*  
CSP:  $1.5\text{mm} \times 1.0\text{mm}$   
WSN:  $2\text{mm} \times 2\text{mm}$



Copyright © 2017, Texas Instruments Incorporated
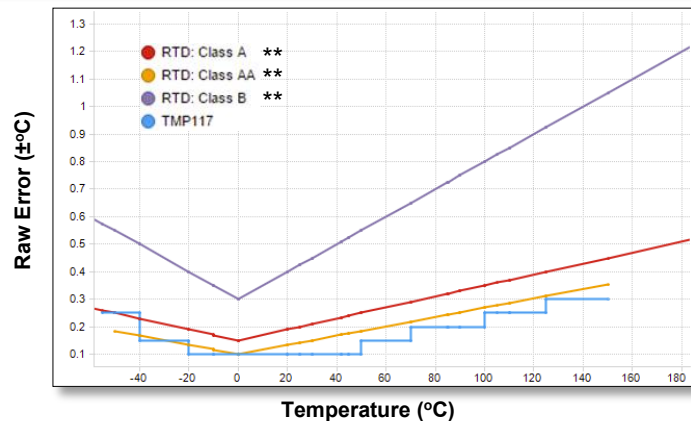
## Challenges with RTD

- Change in resistance is very small, which requires high precision components & AFE to achieve high accuracy.
- High cost of components
  - Platinum RTDs are expensive, other materials used are less accurate
  - Precision Bias & reference resistor network, current reference, amplifier, ADC
- Complex system design requiring precision matched traces, kelvin connections, and/or chopping circuits
- Complex error analysis due to the high number of contributing components. (RTD, resistors, amp, ADC, current source)
- Annual calibration



\*\*Raw Error: Does not include error of additional circuitry for RTDs. TMP117 does not require additional circuitry



TEXAS INSTRUMENTS



# Electrochemical Sensing



TEXAS INSTRUMENTS

# Electrochemical Sensing: Overview

## Block Diagram

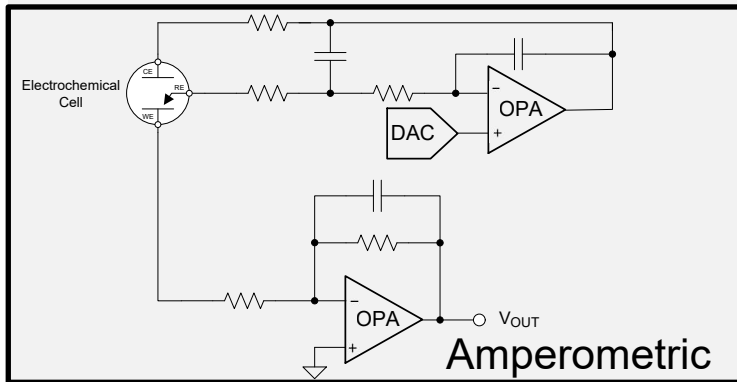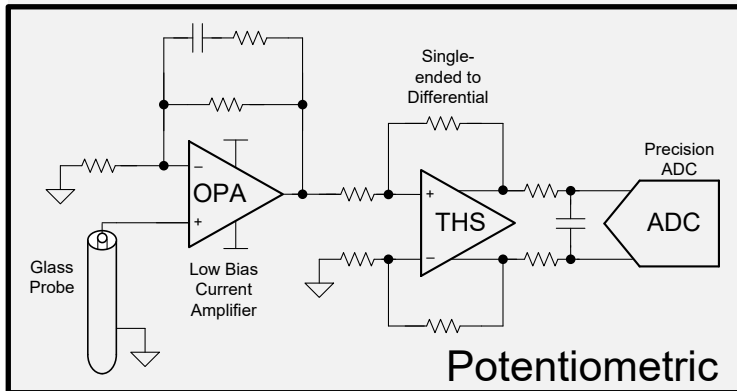

## System Design Challenge

**Design Challenge:** Accurate detection of low voltages and currents to measure blood gases, pH and electrolytes using Potentiometric and Amperometric measurements.

**Solution:** A low noise and high accuracy (including low I<sub>bias</sub> and drifts) analog front ends are essential for accuracy & reliability. The OPA392 is used to measure low currents (100uA-100nA) for the Amperometric measurement.


## Key Devices + Collateral

| Parameter      | Low Offset and Bias Current Amplifiers  | Fully Differential Amplifiers                     | Precision Analog-to-Digital Converters                | Digital-to-Analog Converters   |
|----------------|---|---|---|--|
| GPN            | <a href="#">OPA192</a><br><a href="#">OPA140</a><br><a href="#">LMP91200</a>  | <a href="#">THP210</a><br><a href="#">THP4551</a> | <a href="#">ADS127L01</a><br><a href="#">ADS8900B</a> | <a href="#">DAC60501</a><br><a href="#">DAC70501</a><br><a href="#">DAC80501</a> |
| Description    | Low I <sub>B</sub> , Low noise precision amplifiers   | Low noise, fast transient response FDAs           | Wide Bandwidth, High Resolution ADCs                  | Small 12–16 bit DACs with multiple channel options                               |
| MPM Collateral | <ul style="list-style-type: none"><li><a href="#">In-Vitro Diagnostics EERD</a></li><li><a href="#">Sensor Front Ends</a></li></ul> |   |   |  |

# Motor/Motion Control

# Motion/Motor Control: Overview

## Block Diagram

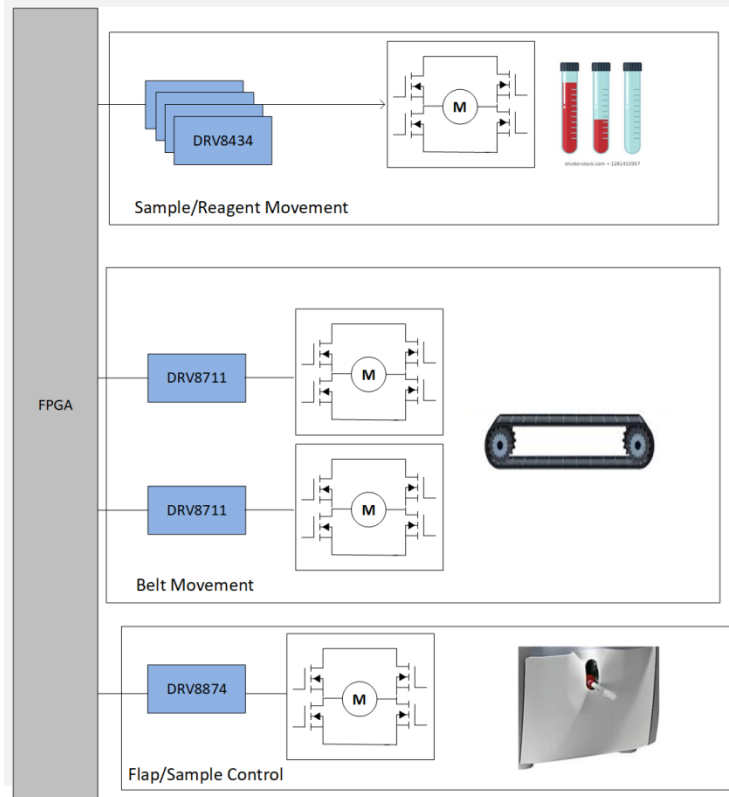

## System Design Challenge

**Design Challenge:** In larger laboratory equipment, there are multiple motor opportunities to move different reagents into the sample and move the sample throughout the system. Increased ease of use, cost and size helps the customer replace external modules.

**Solution:** With 24V/36V/48V rails, 3-5A, stepper or brushed opportunities: integrated fets are preferred for ease of designing while external fets are preferred for higher current ratings. Using the DRV8711 with external fets, with the 1/256 micro-stepping, allows for a more precise distribution of reagents and samples in these systems.

## Key Devices + Collateral

| Parameter      | Discrete  | Discrete   | Discrete  |
|----------------|---|--|---|
| GPN            | <a href="#">DRV8711</a>   | <a href="#">DRV8434</a> (50V)<br><a href="#">DRV8424</a> (35V)           | <a href="#">DRV8876</a><br><a href="#">DRV8874</a><br><a href="#">DRV8873</a> |
| Application    | Belt movement   | Test tube/plates/samples positioning                                     | Sample slots  |
| Description    | 52-V, bipolar stepper motor gate driver with 1/256 microstepping & stall detect   | 50V/35V, 2.5A FS with 1/256 microstepping and integrated current sensing | 37V, 3.5/5/10A brushed driver with integrated current sensing                 |
| MPM Collateral | <a href="#">Understanding Smart Gate Drive</a><br><a href="#">Methods to Configure Current Regulation for Brushed and Stepper Motors (Rev. B)</a> |  |   |



TEXAS INSTRUMENTS



# DRV84xx Family

Industry's smallest P2P Family of stepper motor drivers with best in class motion control



## Integrated Current sensing

Eliminates ***all*** current sense resistors while providing accurate current regulation (*Maximum integration*)

### Benefits

- ✓ **BOM reduction:** Removed sense resistors and reduced board size
- ✓ **Power management:** No power loss over the sense resistor
- ✓ **Easy design:** Hassle-free layout with no sense routing

[More info](#)

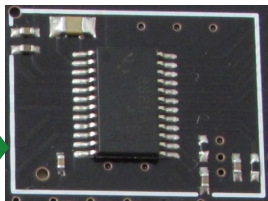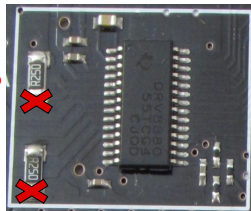


## Smart Tune

Tune Stepper motors effortlessly & automatically (*TI Patented*)

### Benefits

- ✓ **Seamless, quiet tuning:** Motor runs quietly without losing regulation
- ✓ **Power management:** Motor runs more efficiently than fixed decay modes
- ✓ **Shorter design cycle:** No need to spend months tweaking decay modes of motors
- ✓ **Reliability:** auto adjustment to motor parameters over lifetime
- ✓ **Thermal management:** makes system 5-12 degrees cooler than traditional decay modes
- ✓ **Ripple control:** automatically adjusts and controls the ripple current level resulting in higher average torque at each step

[More info;](#) [slides](#)

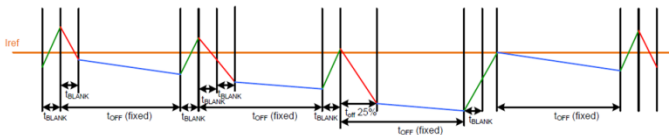

## High Microstepping & more

1/256 Microstepping (*Industry highest*) with (*Industry best*) accuracy of current sense, wide input voltage, low Rdson and protection features

### Benefits

- ✓ **Fine microstepping:** 1/256 microstepping for more accurate and controlled motion
- ✓ **Current Sense Accuracy to  $\pm <5\%$**
- ✓ **5 level protection:** UVLO, CPUV, OCP, OL, OTSD
- ✓ **P2P scalability in QFN reducing size:**
  - ✓ **Smallest 16 Pin TSSOT 3x3mm Package** (1.5m $\Omega$ )
  - ✓ **P2P 4x4mm QFN** package with range of RDson options (0.3 $\Omega$  – 1.2 $\Omega$ )
- ✓ **Flexibility:**
  - Wide operating voltage range (4V - 48V)
  - Simple STEP/DIR interface and EN/PH interface



3.0x3.0mm, 16-pin  
QFN package

# Resources

# In-Vitro Diagnostics Resources on TI.com

| Precision Optical  | High Speed Optical   | Impedance Spectroscopy  |
|--|--|---|
| <ul style="list-style-type: none"><li>• <a href="#">DDC11xEVM-PDK Eval Board</a></li><li>• <a href="#">DDC112 Datasheet</a></li><li>• <a href="#">OPAx392 Product Page</a></li><li>• <a href="#">Resolution-Boosting ADS7066 Using Programmable Averaging Filter</a></li></ul>                   | <ul style="list-style-type: none"><li>• <a href="#">High speed ADCs and Amplifiers for Flow Cytometry</a></li><li>• <a href="#">Flow Cytometry PSPICE Simulation</a></li><li>• <a href="#">Photodiode Amplifier Design</a></li><li>• <a href="#">Why Oversample when Undersampling can do the Job?</a></li><li>• <a href="#">Understanding JESD204B Subclasses and Deterministic Latency</a></li></ul> | <ul style="list-style-type: none"><li>• <a href="#">Impedance Spectroscopy Simulation (Differential)</a></li><li>• <a href="#">Impedance Spectroscopy Simulation (Single-Ended)</a></li></ul>   |
| Thermoelectric Cooling   | Electrochemical Sensing  | Motor Automation  |
| <ul style="list-style-type: none"><li>• <a href="#">Driving a Peltier Element (TEC) Reference Design</a></li><li>• <a href="#">Low Power TEC Driver Reference Design</a></li><li>• <a href="#">Smart AFE Overview Video</a></li><li>• <a href="#">TEC Control with Smart AFE Video</a></li></ul> | <ul style="list-style-type: none"><li>• <a href="#">Sensor Front Ends</a></li><li>• <a href="#">OPA192 Datasheet</a></li><li>• <a href="#">ADS127L01 Product Page</a></li><li>• <a href="#">Fundamentals of Precision ADC Noise Analysis</a></li></ul>   | <ul style="list-style-type: none"><li>• <a href="#">DRV8711 Product Page</a></li><li>• <a href="#">Understanding Smart Gate Drive</a></li><li>• <a href="#">Methods to Configure Current Regulation for Brushed and Stepper Motors (Rev. B)</a></li></ul> |

# Questions?